

实验名称：___Card___ 姓名：___ 学号：___

浙江大学



本科实验报告

装
订
线

姓名：_____

学院： 生物医学工程与仪器科学学院

系： 生物医学工程系

专业： 生物医学工程

学号：_____

指导教师： 余锋

实验名称： Card 姓名： 学号：

专业： 生物医学工程
姓名：
学号：
日期： 2025.5.13
地点： 教 6—204

浙江大学实验报告

课程名称： 硬件描述语言 指导老师： 余锋 实验名称： HDL 实验五

- 一、实验要求
- 二、实验代码与注释
- 三、仿真结果与分析
- 四、讨论与心得

一、实验要求

玩家每次取一张牌，2~10 的牌取值与面值相同，J，Q，K 面值也是 10，A 代表 1。即简化为每次输入点数为 1—10，出现概率相同，测试文件中使用\$random 产生。当总点数小于 18 点就继续叫牌，当总点数超过 21 点时算输，当总点数在[18，21]之间时算胜利。

要求完成：

- 1、画出状态机的状态转换图
- 2、 game_fsm.v

模块要求输入输出信号如下

input clk_i, 时钟输入，100MHz
input rst_i, 高电平复位信号
input card_rdy_i, 取牌 ready 信号，该信号为高时读入 card_value_i
input [3:0] card_value_i, 牌面值，取值为 1—10
output reg card_req_o, 叫牌请求
output reg lost_o, 高电平代表游戏输
output reg [4:0] count_o, 输出此时点数
output reg win_o 高电平代表游戏赢

- 3、 tb_game_fsm.v

实验名称： Card 姓名： 学号：

使用 task 产生仿真激励，信号变化与时钟上升沿对齐，且在玩家叫牌时才会产生新的测试输入。

4、拓展（不做要求）：两个玩家一起玩游戏（例化两个 game_fsm，添加裁判模块）。

游戏过程举例：

- (1) 两个玩家准备就绪，裁判宣布开始游戏。
- (2) 游戏开始时，双方点数为 0，开始叫牌，裁判把牌轮流分配给两个玩家。
- (3) 玩家拿到牌后计算当前点数，根据当前点数选择继续叫牌或停止叫牌。
- (4) 当一方停止叫牌，另一方仍然叫牌时，裁判只发牌给叫牌方。
- (5) 当两方都停止叫牌后，游戏结束，裁判给出胜负结果。

二、实验代码与注释

（一）一名玩家

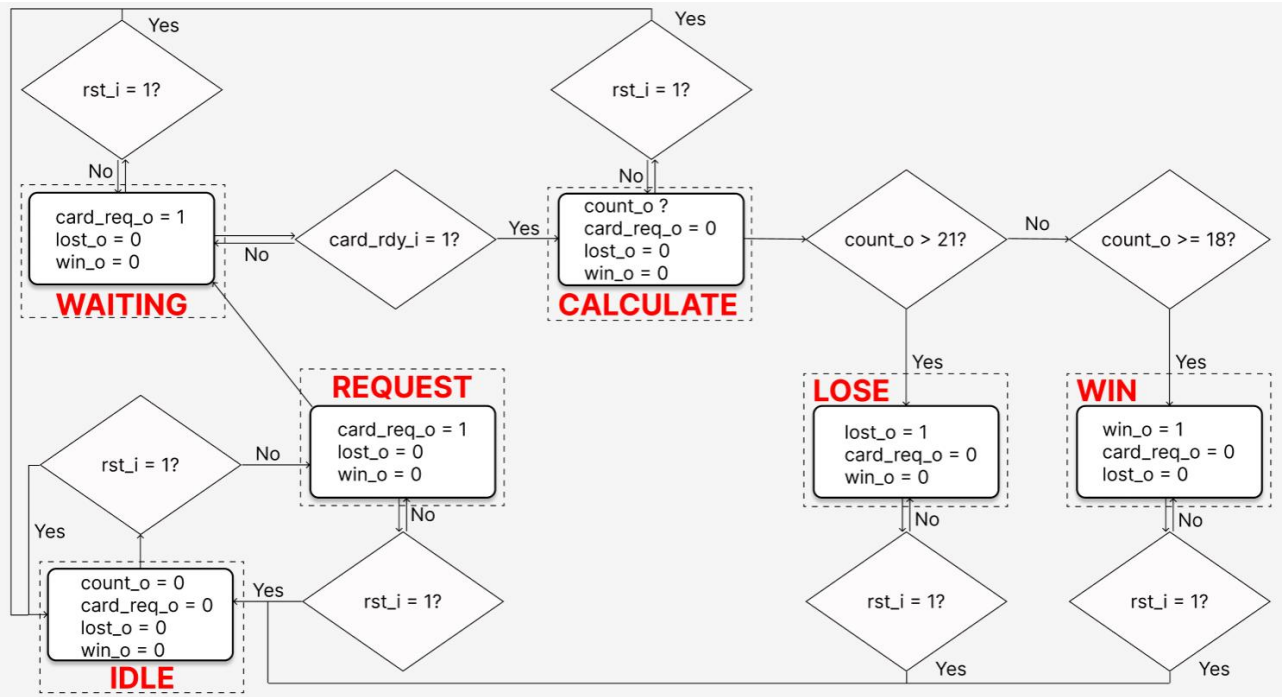


图 1 ASM 状态转移图

1、game_fsm.v

```
01 定义：
02 状态 S = {IDLE, REQUEST_CARD, WAIT_CARD, CALCULATE, WIN, LOSE}
03 输入信号 I = {clk, rst, card_rdy, card_value}
```

实验名称：___Card___ 姓名：___ 学号：___

```

04      输出信号 O = {card_req, lost, count, win}
05      内部寄存器 R = {card_rdy_reg, card_value_reg, current_state,
06 next_state}
07
08 // 状态转换算法（组合逻辑部分）
09 ALGORITHM StateTransition(current_state)
10     // 默认输出
11     next_state ← current_state
12     card_req ← 0
13     lost ← 0
14     win ← 0
15
16     CASE current_state OF
17         IDLE:
18             next_state ← REQUEST_CARD
19
20         REQUEST_CARD:
21             card_req ← 1
22             next_state ← WAIT_CARD
23
24         WAIT_CARD:
25             card_req ← 1 // 保持请求直到收到卡牌
26             IF card_rdy_reg = 1 THEN
27                 next_state ← CALCULATE
28             ENDIF
29
30         CALCULATE:
31             IF count > 21 THEN
32                 next_state ← LOSE
33             ELSE IF count ≥ 18 AND count ≤ 21 THEN
34                 next_state ← WIN
35             ELSE // count < 18
36                 next_state ← REQUEST_CARD
37             ENDIF
38
39         WIN:
40             win ← 1
41             // 保持在 WIN 状态直到复位
42
43         LOSE:
44             lost ← 1
45             // 保持在 LOSE 状态直到复位
46
47     ENDCASE

```

实验名称: Card 姓名: 学号:

```

48     RETURN next_state, card_req, lost, win
49
50 // 时序逻辑算法
51 ALGORITHM SequentialLogic(clk, rst)
52     ON RISING_EDGE(clk) OR RISING_EDGE(rst):
53         IF rst = 1 THEN
54             current_state ← IDLE
55             count ← 0
56             card_rdy_reg ← 0
57             card_value_reg ← 无效值
58         ELSE
59             // 捕获输入信号
60             card_rdy_reg ← card_rdy
61             IF card_rdy = 1 THEN
62                 card_value_reg ← card_value
63             ELSE
64                 card_value_reg ← 无效值
65             ENDIF
66
67             // 更新状态
68             current_state ← next_state
69
70             // 计分逻辑
71             IF current_state = WAIT_CARD AND card_rdy_reg = 1 THEN
72                 IF card_value_reg ≥ 1 AND card_value_reg ≤ 10 THEN
73                     count ← count + card_value_reg
74                 ENDIF
75             ENDIF
76         ENDIF

```

```

module game_fsm (
    input          clk_i,
    input          rst_i,
    input          card_rdy_i,
    input [3:0]    card_value_i,
    output reg     card_req_o,
    output reg     lost_o,
    output reg [4:0] count_o,
    output reg     win_o
);

// State definition
localparam IDLE = 3'b000;

```

实验名称: Card 姓名: 学号:

```

localparam REQUEST_CARD = 3'b001;
localparam WAIT_CARD    = 3'b010;
localparam CALCULATE     = 3'b011;
localparam WIN           = 3'b100;
localparam LOSE          = 3'b101;
reg [2:0] current_state;
reg [2:0] next_state;
// Internal signals for registered inputs
reg card_rdy_reg;          // Registered version of card_rdy_i
reg [3:0] card_value_reg;  // Registered version of card_value_i, captured
                           // when card_rdy_i is high
always @(*) begin
    next_state = current_state;
    card_req_o = 1'b0;
    lost_o = 1'b0;
    win_o = 1'b0;
    case (current_state)
        IDLE: begin
            next_state = REQUEST_CARD;
        end
        REQUEST_CARD: begin
            card_req_o = 1'b1;
            next_state = WAIT_CARD;
        end
        WAIT_CARD: begin
            card_req_o = 1'b1; // Keep requesting until card is ready
            if (card_rdy_reg) begin // Use registered card_rdy_reg
                next_state = CALCULATE;
            end else begin
                next_state = WAIT_CARD;
            end
        end
        CALCULATE: begin
            // card_req_o is 0 by default
            if (count_o > 5'd21) begin
                next_state = LOSE;
            end else if (count_o >= 5'd18 && count_o <= 5'd21) begin
                next_state = WIN;
            end else if (count_o < 5'd18) begin
                next_state = REQUEST_CARD;
            end else begin // Should not happen given the conditions above
                next_state = IDLE; // Safety default
            end
        end
    end
end

```

实验名称: Card 姓名: 学号:

```

    WIN: begin
        win_o = 1'b1;
        next_state = WIN; // Stay in WIN until reset
    end
    LOSE: begin
        lost_o = 1'b1;
        next_state = LOSE; // Stay in LOSE until reset
    end
    default: begin
        next_state = IDLE;
    end
endcase
end

// Sequential logic for state transition and count update
always @(posedge clk_i or posedge rst_i) begin
    if (rst_i) begin
        current_state <= IDLE;
        count_o <= 5'd0;
        card_rdy_reg <= 1'b0; // Reset registered input
        card_value_reg <= 4'bz; // Reset registered input to an invalid state

    end else begin
        // Capture inputs first
        card_rdy_reg <= card_rdy_i;
        if (card_rdy_i) begin
            card_value_reg <= card_value_i;
        end else begin
            card_value_reg <= 4'bz; // Keep it invalid if card_rdy_i is Low
        end
        current_state <= next_state; // current_state updates based on
        next_state from previous cycle's inputs (via _reg)
        $display("FSM_SEQ @%t: clk=%b, rst=%b, current_state_REG=%h,
        next_state_COMB=%h, card_rdy_i(input)=%b, card_value_i(input)=%d,
        card_rdy_reg(old)=%b, card_value_reg(old)=%d, count_o_REG_OLD=%d",
            $time, clk_i, rst_i, current_state, next_state, card_rdy_i,
            card_value_i, card_rdy_reg, card_value_reg, count_o);
        // Accumulate count based on registered inputs from the previous cycle
        if (current_state == WAIT_CARD && card_rdy_reg) begin
            if (card_value_reg > 0 && card_value_reg <= 10) begin
                count_o <= count_o + card_value_reg;
                $display("FSM_SEQ @%t: ACCUMULATING! count_o <= %d + %d
                (using card_value_reg). New count will be %d", $time, count_o, card_value_reg,
                count_o + card_value_reg);
            end else begin

```

实验名称: Card 姓名: 学号:

```

        $display("FSM_SEQ @%t: card_value_reg invalid (%d) or
card_rdy_reg low, not accumulating.", $time, card_value_reg);
    end
    end else if (next_state == IDLE && current_state != IDLE) begin
        // Reset count if moving to IDLE
        count_o <= 5'd0;
        $display("FSM_SEQ @%t: RESETTNG count_o to 0 (transition to IDLE
from %h)", $time, current_state);
    end
    // WIN/LOSE states: count_o holds its value, handled by no assignment
    here unless resetting.
end
endmodule

```

2、tb_game_fsm.v

```

01 ALGORITHM TestBenchGameFSM()
02     // 初始化
03     clk <- 0
04     rst <- 1
05     card_rdy <- 0
06     card_value <- 无效值
07
08     // 设置随机数种子
09     seed <- 设定值或当前时间
10
11     // 生成时钟
12     PARALLEL PROCESS ClockGeneration():
13         FOREVER:
14             WAIT(5ns)
15             clk <- NOT clk
16
17     // 提供卡牌任务
18     PROCEDURE ProvideCard():
19         WAIT_FOR(RISING_EDGE(clk))
20         IF card_req = 1 THEN
21             random_val <- RANDOM() MOD 10 + 1 // 生成 1-10 范围的随机数
22             card_value <- random_val
23             card_rdy <- 1
24
25             WAIT_FOR(RISING_EDGE(clk))
26             card_rdy <- 0

```


实验名称：___Card___ 姓名：___ 学号：___

```

27         card_value ← 无效值
28
29         PRINT("提供卡牌值:", random_val)
30     ENDIF
31
32     // 主测试序列
33     MAIN:
34         // 施加复位
35         WAIT(20ns)
36         rst ← 0
37
38         // 游戏循环
39         FOR i = 1 TO MAX_ITERATIONS DO
40             IF win = 1 OR lost = 1 THEN
41                 IF win = 1 THEN PRINT("游戏获胜! 最终点数:", count)
42                 IF lost = 1 THEN PRINT("游戏失败! 最终点数:", count)
43
44                 // 重置游戏
45                 rst ← 1
46                 WAIT(20ns)
47                 rst ← 0
48             ENDIF
49
50             IF card_req = 1 THEN
51                 ProvideCard()
52             ELSE
53                 WAIT_FOR(RISING_EDGE(clk))
54             ENDIF
55         ENDFOR
56
57         PRINT("仿真结束")
58         FINISH()

```

```

`timescale 1ns / 1ps

module tb_game_fsm;
// Inputs
reg clk_i;
reg rst_i;
reg card_rdy_i;
reg [3:0] card_value_i;
reg [31:0] temp_rand;    // Temporary variable for $random
// Outputs

```

实验名称: Card 姓名: 学号:

```

wire card_req_o;
wire lost_o;
wire [4:0] count_o;
wire win_o;
game_fsm uut (
    .clk_i(clk_i),
    .rst_i(rst_i),
    .card_rdy_i(card_rdy_i),
    .card_value_i(card_value_i),
    .card_req_o(card_req_o),
    .lost_o(lost_o),
    .count_o(count_o),
    .win_o(win_o)
);
// Seed for random number generator
initial begin
    temp_rand = 12345; // Assign seed value to variable
    temp_rand = $time;
    temp_rand = $random(temp_rand); // Set seed properly
end
// Clock generation
initial begin
    clk_i = 0;
    forever #5 clk_i = ~clk_i; // 100MHz clock
end
// Task to provide a card
task provide_card;
    reg [3:0] provided_value; // To store the value for display
    begin
        // P0: card_req_o observed high by testbench.
        // FSM state could be REQUEST_CARD or WAIT_CARD (if it looped back).
        @(posedge clk_i); // Sync to P1. FSM updates its state based on P0
        values.
        // If FSM was REQUEST_CARD, it transitions to
        WAIT_CARD here.
        // If FSM was WAIT_CARD, it stays WAIT_CARD (as
        card_rdy_i was low at P0 edge).
        if (card_req_o) begin // card_req_o should still be high if FSM is
        in WAIT_CARD.
            temp_rand = $random;
            provided_value = (temp_rand % 10);
            if (provided_value < 0) provided_value = provided_value + 10; //
            Ensure 0-9 if % is negative
            provided_value = provided_value + 1; // Shift to 1-10 range
        end
    end
endtask

```

实验名称: Card 姓名: 学号:

```

        card_value_i = provided_value;
        card_rdy_i = 1'b1;
        // card_value_i and card_rdy_i are now set. FSM will sample these
        // at the P2 edge.
        @(posedge clk_i); // Sync to P2.
        // At this P2 edge, FSM (which was in WAIT_CARD
        // at P1 start)
        // samples card_value_i and card_rdy_i (which
        // is 1'b1).
        // It should update count_o and transition to
        CALCULATE.
        card_rdy_i = 1'b0; // De-assert card_rdy_i *after* FSM has used
        // it at P2 and after the #1 delay.
        card_value_i = 4'bz;
        $display("Provided card: %d at time %t. FSM state (after P2
        processing): %h. New count: %d",
        provided_value, $time, uut.current_state, count_o);
    end else begin
        $display("TB: At %t (P1 edge), FSM card_req_o went low
        unexpectedly. No card provided.", $time);
    end
end
endtask
// Test sequence
initial begin
    // Initialize Inputs
    rst_i = 1'b1;
    card_rdy_i = 1'b0;
    card_value_i = 4'bz;
    // Apply reset
    #20;
    rst_i = 1'b0;
    $display("Reset released at time %t", $time);
    // Game simulation loop
    repeat (70) begin // Max 70 cards, or until game ends
        if (win_o || lost_o) begin
            if (win_o) $display("Game WIN! Final count: %d at time %t",
            count_o, $time);
            if (lost_o) $display("Game LOST! Final count: %d at time %t",
            count_o, $time);

            // Reset for a new game
            rst_i = 1'b1;

```

实验名称: Card 姓名: 学号:

```

        card_rdy_i = 1'b0;
        card_value_i = 4'bz;
        #20;
        rst_i = 1'b0;
        $display("New game started after reset at time %t", $time);
    end

    if (card_req_o) begin
        provide_card();
    end else begin
        @(posedge clk_i); // If not requesting, just wait for next cycle
    end
end
$display("Simulation finished after multiple attempts or timeout at
time %t", $time);
$finish;
end
// Monitor changes
initial begin
    $monitor("Time=%t, clk=%b, rst=%b, card_req=%b, card_rdy=%b,
card_val=%d, count=%d, win=%b, lost=%b, state=%h",
        $time, clk_i, rst_i, card_req_o, card_rdy_i, card_value_i,
count_o, win_o, lost_o, uut.current_state);
    $dumpfile("tb_game_fsm.vcd");
    $dumpvars(0, tb_game_fsm);
    #20000 $finish; // Increased simulation time, e.g., to 2000ns
end
endmodule

```

(二) 二名玩家

1、referee.v

```

module referee (
    input          clk_i,
    input          rst_i,

    // 玩家1 接口
    input          p1_card_req_i,
    output reg     p1_card_rdy_o,
    output reg [3:0] p1_card_value_o,
    input          p1_win_i,
    input          p1_lost_i,
    input [4:0]    p1_count_i,

```

实验名称: Card 姓名: 学号:

```
// 玩家2 接口
input          p2_card_req_i,
output reg     p2_card_rdy_o,
output reg [3:0] p2_card_value_o,
input          p2_win_i,
input          p2_lost_i,
input [4:0]     p2_count_i,

// 游戏结果输出
output reg [1:0] game_result_o // 00: 未结束, 01: 玩家1 胜, 10: 玩家
2 胜, 11: 平局
);

// 状态定义
localparam INIT          = 3'b000; // 初始状态
localparam PLAYER1_TURN = 3'b001; // 玩家1 回合
localparam PLAYER2_TURN = 3'b010; // 玩家2 回合
localparam DEAL_CARD    = 3'b011; // 发牌状态
localparam JUDGE_RESULT = 3'b100; // 判定结果
reg [2:0] current_state;
reg [2:0] next_state;
reg [3:0] card_to_deal; // 即将发出的牌值
reg       turn_flag;    // 0: 玩家1 回合, 1: 玩家2 回合
// 随机数生成
reg [31:0] rand_temp;
always @(posedge clk_i) begin
    if (current_state == DEAL_CARD) begin
        rand_temp = $random;
        card_to_deal <= (rand_temp % 10) + 1;
        if (card_to_deal > 10 || card_to_deal < 1) begin
            card_to_deal <= (rand_temp[3:0] % 10) + 1; // 备选随机方案
        end
    end
end
// 组合逻辑部分: 状态转换和输出
always @(*) begin
    // 默认值
    next_state = current_state;
    p1_card_rdy_o = 1'b0;
    p2_card_rdy_o = 1'b0;
    p1_card_value_o = 4'b0;
    p2_card_value_o = 4'b0;
```

实验名称：___Card___ 姓名：___ 学号：___

```

case (current_state)
  INIT: begin
    // 初始化后转到玩家1 回合
    next_state = PLAYER1_TURN;
  end

  PLAYER1_TURN: begin
    if (p1_card_req_i && !p1_win_i && !p1_lost_i) begin
      // 玩家1 请求牌, 转到发牌状态
      next_state = DEAL_CARD;
    end else if (!p1_card_req_i || p1_win_i || p1_lost_i) begin
      // 玩家1 不要牌或已经完成游戏
      next_state = PLAYER2_TURN;
    end
  end

  PLAYER2_TURN: begin
    if (p2_card_req_i && !p2_win_i && !p2_lost_i) begin
      // 玩家2 请求牌, 转到发牌状态
      next_state = DEAL_CARD;
    end else if (!p2_card_req_i || p2_win_i || p2_lost_i) begin
      // 检查是否需要回到玩家1
      if (p1_card_req_i && !p1_win_i && !p1_lost_i) begin
        next_state = PLAYER1_TURN;
      end else if ((!p1_card_req_i || p1_win_i || p1_lost_i) &&
        (!p2_card_req_i || p2_win_i || p2_lost_i))
      begin
        // 两位玩家都不再请求牌或已经完成游戏
        next_state = JUDGE_RESULT;
      end else begin
        // 保持在玩家2 回合
        next_state = PLAYER2_TURN;
      end
    end
  end

  DEAL_CARD: begin
    if (turn_flag == 1'b0) begin
      // 发牌给玩家1
      p1_card_rdy_o = 1'b1;
      p1_card_value_o = card_to_deal;
      next_state = PLAYER2_TURN; // 发完牌后转到玩家2 回合
    end else begin
      // 发牌给玩家2

```

实验名称：___Card___ 姓名：___ 学号：___

```

        p2_card_rdy_o = 1'b1;
        p2_card_value_o = card_to_deal;
        next_state = PLAYER1_TURN; // 发完牌后转到玩家1 回合
    end
end

JUDGE_RESULT: begin
    // 保持在当前状态，等待复位
    next_state = JUDGE_RESULT;
end

default: begin
    next_state = INIT;
end
endcase
end
// 时序逻辑部分：状态更新和输出寄存器
always @(posedge clk_i or posedge rst_i) begin
    if (rst_i) begin
        current_state <= INIT;
        turn_flag <= 1'b0; // 初始为玩家1 回合
        game_result_o <= 2'b00;
    end else begin
        current_state <= next_state;

        // 更新回合标志
        if (current_state == DEAL_CARD) begin
            turn_flag <= ~turn_flag;
        end

        // 判定游戏结果
        if (current_state == JUDGE_RESULT) begin
            if (p1_lost_i && !p2_lost_i) begin
                // 玩家1 爆牌，玩家2 未爆牌，玩家2 胜
                game_result_o <= 2'b10;
            end else if (!p1_lost_i && p2_lost_i) begin
                // 玩家1 未爆牌，玩家2 爆牌，玩家1 胜
                game_result_o <= 2'b01;
            end else if (p1_lost_i && p2_lost_i) begin
                // 两人都爆牌，平局
                game_result_o <= 2'b11;
            end else begin
                // 两人都未爆牌，比点数
                if (p1_count_i > p2_count_i) begin

```

实验名称：___Card___ 姓名：___ 学号：___

```

        game_result_o <= 2'b01; // 玩家1 胜
    end else if (p1_count_i < p2_count_i) begin
        game_result_o <= 2'b10; // 玩家2 胜
    end else begin
        game_result_o <= 2'b11; // 平局
    end
end
end
end
end
endmodule

```

2、two_player_game.v

```

module referee (
    input          clk_i,
    input          rst_i,

    // 玩家1 接口
    input          p1_card_req_i,
    output reg     p1_card_rdy_o,
    output reg [3:0] p1_card_value_o,
    input          p1_win_i,
    input          p1_lost_i,
    input [4:0]    p1_count_i,

    // 玩家2 接口
    input          p2_card_req_i,
    output reg     p2_card_rdy_o,
    output reg [3:0] p2_card_value_o,
    input          p2_win_i,
    input          p2_lost_i,
    input [4:0]    p2_count_i,

    // 游戏结果输出
    output reg [1:0] game_result_o // 00: 未结束, 01: 玩家1 胜, 10: 玩家
2 胜, 11: 平局
);

// 状态定义
localparam INIT          = 3'b000; // 初始状态
localparam PLAYER1_TURN = 3'b001; // 玩家1 回合
localparam PLAYER2_TURN = 3'b010; // 玩家2 回合
localparam DEAL_CARD    = 3'b011; // 发牌状态

```


实验名称：___Card___ 姓名：___ 学号：___

```

localparam JUDGE_RESULT = 3'b100; // 判定结果
reg [2:0] current_state;
reg [2:0] next_state;
reg [3:0] card_to_deal; // 即将发出的牌值
reg      turn_flag; // 0: 玩家1 回合, 1: 玩家2 回合
// 随机数生成
reg [31:0] rand_temp;
always @(posedge clk_i) begin
    if (current_state == DEAL_CARD) begin
        rand_temp = $random;
        card_to_deal <= (rand_temp % 10) + 1;
        if (card_to_deal > 10 || card_to_deal < 1) begin
            card_to_deal <= (rand_temp[3:0] % 10) + 1; // 备选随机方案
        end
    end
end
// 组合逻辑部分：状态转换和输出
always @(*) begin
    // 默认值
    next_state = current_state;
    p1_card_rdy_o = 1'b0;
    p2_card_rdy_o = 1'b0;
    p1_card_value_o = 4'b0;
    p2_card_value_o = 4'b0;

    case (current_state)
        INIT: begin
            // 初始化后转到玩家1 回合
            next_state = PLAYER1_TURN;
        end

        PLAYER1_TURN: begin
            if (p1_card_req_i && !p1_win_i && !p1_lost_i) begin
                // 玩家1 请求牌, 转到发牌状态
                next_state = DEAL_CARD;
            end else if (!p1_card_req_i || p1_win_i || p1_lost_i) begin
                // 玩家1 不要牌或已经完成游戏
                next_state = PLAYER2_TURN;
            end
        end

        PLAYER2_TURN: begin
            if (p2_card_req_i && !p2_win_i && !p2_lost_i) begin
                // 玩家2 请求牌, 转到发牌状态

```

实验名称：___Card___ 姓名：___ 学号：___

```

        next_state = DEAL_CARD;
    end else if (!p2_card_req_i || p2_win_i || p2_lost_i) begin
        // 检查是否需要回到玩家1
        if (p1_card_req_i && !p1_win_i && !p1_lost_i) begin
            next_state = PLAYER1_TURN;
        end else if ((!p1_card_req_i || p1_win_i || p1_lost_i) &&
            (!p2_card_req_i || p2_win_i || p2_lost_i))
begin
        // 两位玩家都不再请求牌或已经完成游戏
        next_state = JUDGE_RESULT;
    end else begin
        // 保持在玩家2 回合
        next_state = PLAYER2_TURN;
    end
end
end

DEAL_CARD: begin
    if (turn_flag == 1'b0) begin
        // 发牌给玩家1
        p1_card_rdy_o = 1'b1;
        p1_card_value_o = card_to_deal;
        next_state = PLAYER2_TURN; // 发完牌后转到玩家2 回合
    end else begin
        // 发牌给玩家2
        p2_card_rdy_o = 1'b1;
        p2_card_value_o = card_to_deal;
        next_state = PLAYER1_TURN; // 发完牌后转到玩家1 回合
    end
end

JUDGE_RESULT: begin
    // 保持在当前状态，等待复位
    next_state = JUDGE_RESULT;
end

default: begin
    next_state = INIT;
end
endcase
end

// 时序逻辑部分：状态更新和输出寄存器
always @(posedge clk_i or posedge rst_i) begin
    if (rst_i) begin

```

实验名称: Card 姓名: 学号:

```

        current_state <= INIT;
        turn_flag <= 1'b0; // 初始为玩家1 回合
        game_result_o <= 2'b00;
    end else begin
        current_state <= next_state;

        // 更新回合标志
        if (current_state == DEAL_CARD) begin
            turn_flag <= ~turn_flag;
        end

        // 判定游戏结果
        if (current_state == JUDGE_RESULT) begin
            if (p1_lost_i && !p2_lost_i) begin
                // 玩家1 爆牌, 玩家2 未爆牌, 玩家2 胜
                game_result_o <= 2'b10;
            end else if (!p1_lost_i && p2_lost_i) begin
                // 玩家1 未爆牌, 玩家2 爆牌, 玩家1 胜
                game_result_o <= 2'b01;
            end else if (p1_lost_i && p2_lost_i) begin
                // 两人都爆牌, 平局
                game_result_o <= 2'b11;
            end else begin
                // 两人都未爆牌, 比点数
                if (p1_count_i > p2_count_i) begin
                    game_result_o <= 2'b01; // 玩家1 胜
                end else if (p1_count_i < p2_count_i) begin
                    game_result_o <= 2'b10; // 玩家2 胜
                end else begin
                    game_result_o <= 2'b11; // 平局
                end
            end
        end
    end
end
endmodule

```

3、tb_two_player_game.v

```

`timescale 1ns / 1ps

module tb_two_player_game;
    // 输入信号
    reg clk_i;

```

实验名称: Card 姓名: 学号:

```
reg rst_i;
// 输出信号
wire [1:0] game_result;
wire [4:0] p1_count;
wire [4:0] p2_count;
wire p1_win;
wire p1_lost;
wire p2_win;
wire p2_lost;
// 统计多局游戏的结果
integer total_games;
integer p1_wins;
integer p2_wins;
integer draws;
integer game_timer;
integer is_timeout;
// 例化待测模块
two_player_game uut (
    .clk_i(clk_i),
    .rst_i(rst_i),
    .game_result_o(game_result),
    .p1_count_o(p1_count),
    .p2_count_o(p2_count),
    .p1_win_o(p1_win),
    .p1_lost_o(p1_lost),
    .p2_win_o(p2_win),
    .p2_lost_o(p2_lost)
);
// 生成时钟信号
initial begin
    clk_i = 0;
    forever #5 clk_i = ~clk_i; // 100MHz 时钟
end
// 测试序列
initial begin
    // 初始化统计数据
    total_games = 0;
    p1_wins = 0;
    p2_wins = 0;
    draws = 0;
    game_timer = 0;

    // 运行多局游戏
    repeat (5) begin // 设置运行5局游戏
```

实验名称: Card 姓名: 学号:

```
// 初始化
rst_i = 1;
is_timeout = 0;

// 复位释放
#20 rst_i = 0;
$display("第%d 局游戏开始, 复位释放于时间 %t", total_games+1, $time);

// 简单的超时检测
game_timer = 0;
while (game_result == 2'b00 && game_timer < 200) begin
    #50 game_timer = game_timer + 1;
end

// 检查是否超时
if (game_result == 2'b00) begin
    $display("第%d 局游戏超时, 强制结束", total_games+1);
    is_timeout = 1;
end else begin
    // 记录游戏结果
    total_games = total_games + 1;

    if (game_result == 2'b01) p1_wins = p1_wins + 1;
    else if (game_result == 2'b10) p2_wins = p2_wins + 1;
    else if (game_result == 2'b11) draws = draws + 1;

    // 显示本局结果
    $display("第%d 局游戏结束于时间 %t", total_games, $time);

    if (game_result == 2'b01) $display("本局结果: 玩家 1 获胜");
    else if (game_result == 2'b10) $display("本局结果: 玩家 2 获胜");
    else if (game_result == 2'b11) $display("本局结果: 平局");

    $display("玩家 1: 点数 = %d, 赢 = %b, 输 = %b", p1_count, p1_win,
p1_lost);
    $display("玩家 2: 点数 = %d, 赢 = %b, 输 = %b", p2_count, p2_win,
p2_lost);
    $display("-----");
end

// 在进入下一局之前等待一段时间
#100;
end
```

实验名称：___Card___ 姓名：___ 学号：___

```
// 显示总体结果
$display("\n===== 游戏统计 =====");
$display("总局数: %0d", total_games);
$display("玩家 1 胜场: %0d", p1_wins);
$display("玩家 2 胜场: %0d", p2_wins);
$display("平局: %0d", draws);
$display("===== \n");

#100 $finish;
end
// 监视信号变化
initial begin
    $monitor("时间=%t, 复位=%b, 结果=%b, 玩家 1(点数=%d, 赢=%b, 输=%b), 玩家 2(点数=%d, 赢=%b, 输=%b)",
        $time, rst_i, game_result, p1_count, p1_win, p1_lost, p2_count,
        p2_win, p2_lost);

    $dumpfile("tb_two_player_game.vcd");
    $dumpvars(0, tb_two_player_game);
end
endmodule
```

装
订
线


三、仿真结果与分析

Gtkwave 的 count_o 为十六进制，【11】（hex）实际上是【17】（dec）。

（一）单名玩家

实验名称： Card 姓名： 学号：


1、第一轮

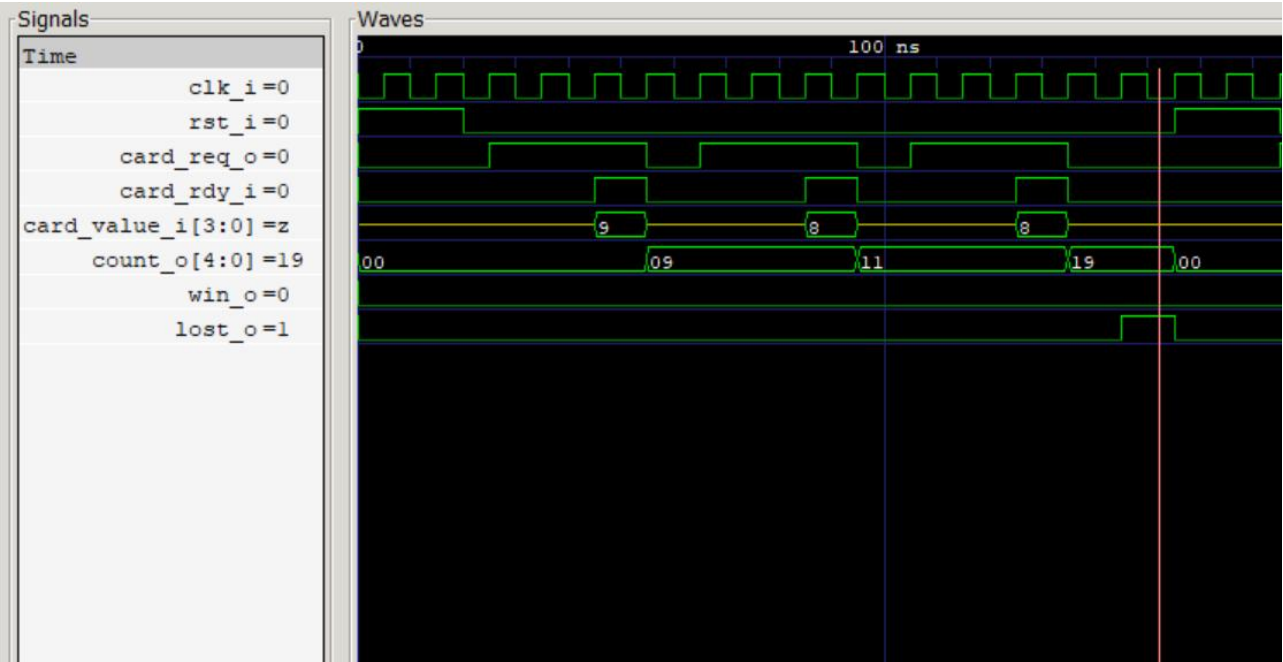

可见 `card_value_i` 随机发牌 3 次，分别为 9、8、8，累积得到的 `count_o` 为 $25 > 21$ ，因此在此 `count_o` 判断结束后的下一个上升沿将其置 1。经过一个时钟周期后 `rst` 置位，开始下一轮游戏。

实验名称： Card 姓名： 学号：


2、第二轮

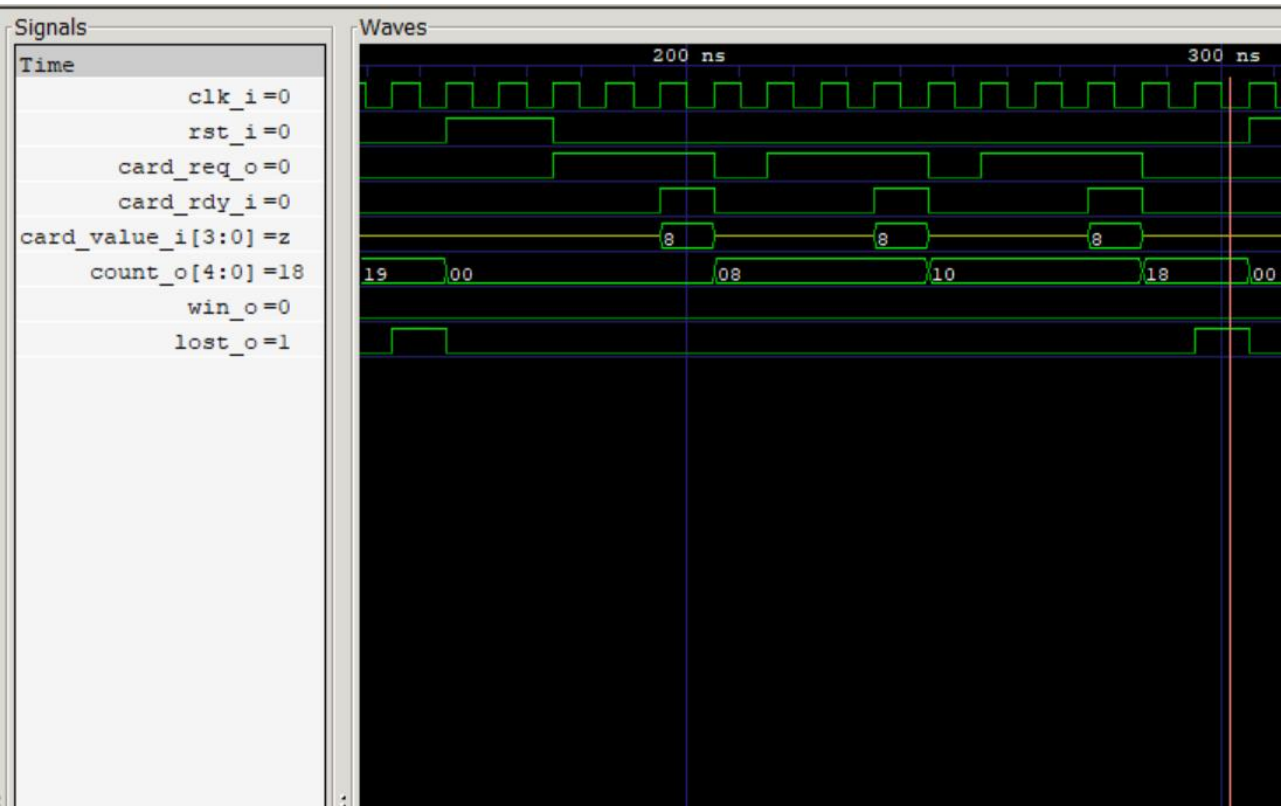

第二轮三次发牌累积得 24>21，依然判负。


实验名称： Card 姓名： 学号：

3、第三轮

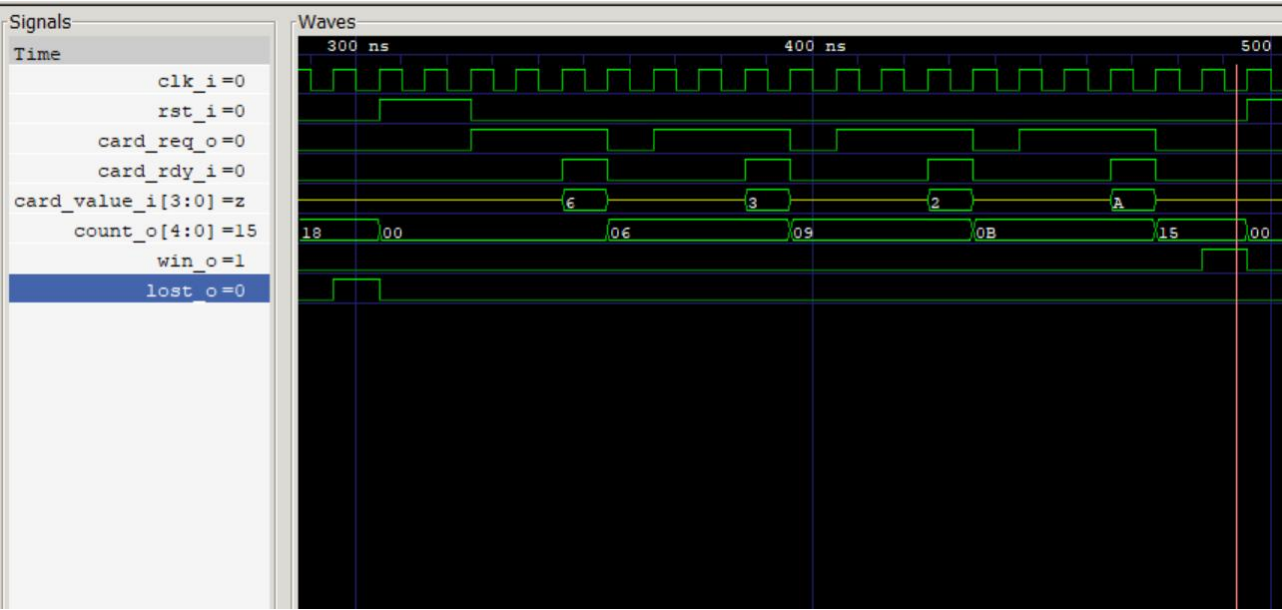

这一轮随机发了 4 次牌才得到最终结果 $21 \in [18, 21]$ ，因此举起 `win_o`。

4、后续二轮

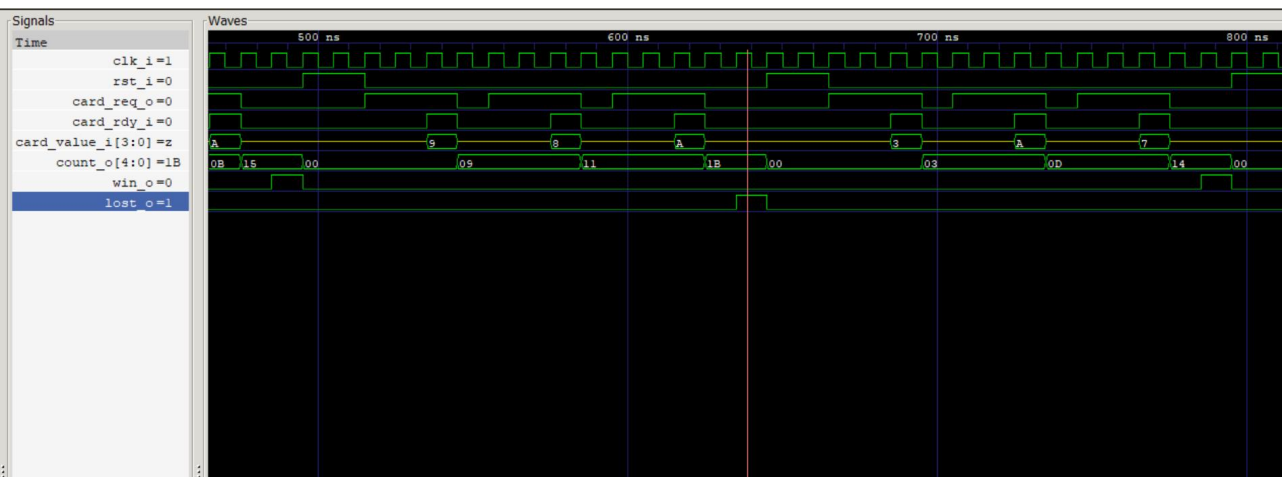

这两轮一次是 27，一次是 20。最后状态转换达到主循环设定 repeat 的上限 70，仿真结束。


(二) 二名玩家

此处使用 `iverilog -g2001 -o two_player_game_tb.vvp edge/tb_two_player_game.v edge/two_player_game.v edge/referee.v game_fsm.v` 来进行编译，也就是将单玩家状态机

实验名称： Card 姓名： 学号：

复用两次并添加裁判模块协调。

1、第一轮

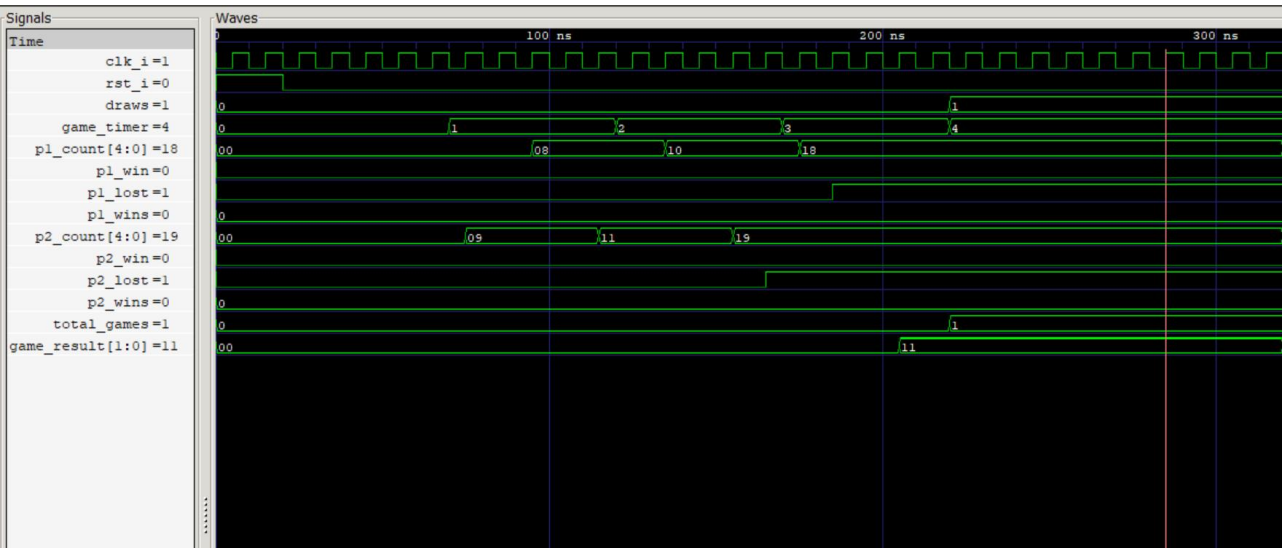


game_timer 用于计时计数，最开始是打算作为超时和发牌数的计时器使用。

玩家 2 (p2) 先获得牌：9 → 17 → 25（爆牌）

玩家 1 (p1) 后获得牌：8 → 16 → 24（爆牌）

两位玩家都爆牌了，分别置位各自的 lost，游戏最终结果 game_result 向量设为 11（二进制），表示平局。

2、第二轮

 


实验名称： Card 姓名： 学号：

玩家 2: 10 → 18

玩家 1: 2 → 11 → 21


是个 win-win 局面，所以 referee 还是判平局。同时 total_games++自增。

3、第三轮

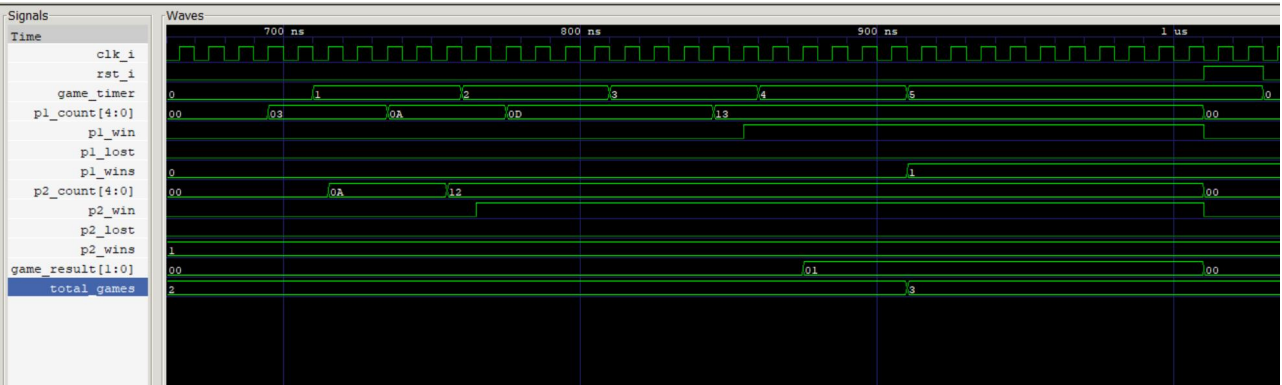


本次是玩家 1 爆牌，因此玩家 2 胜利，game_result<=01。

4、第四轮

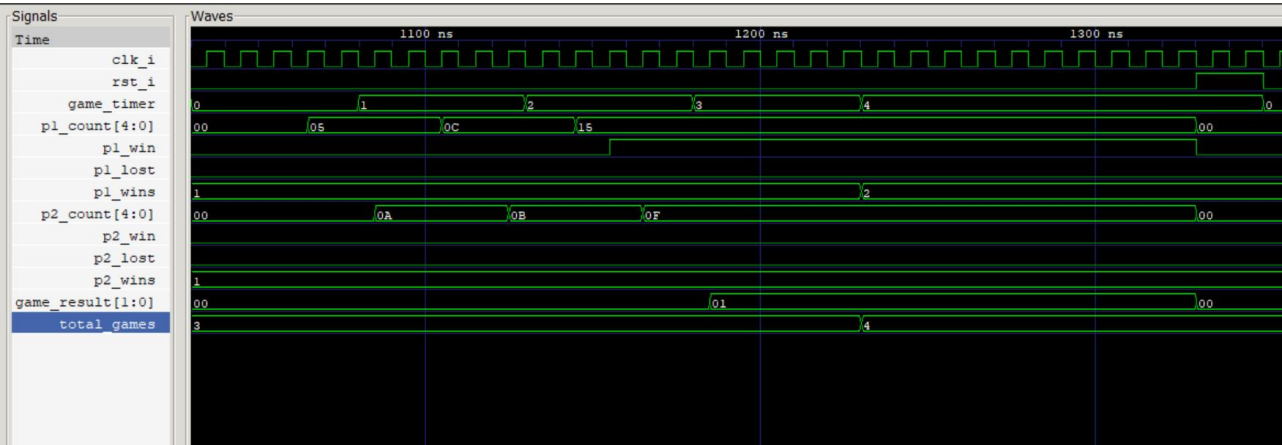

5、第五轮

实验名称： Card 姓名： 学号：

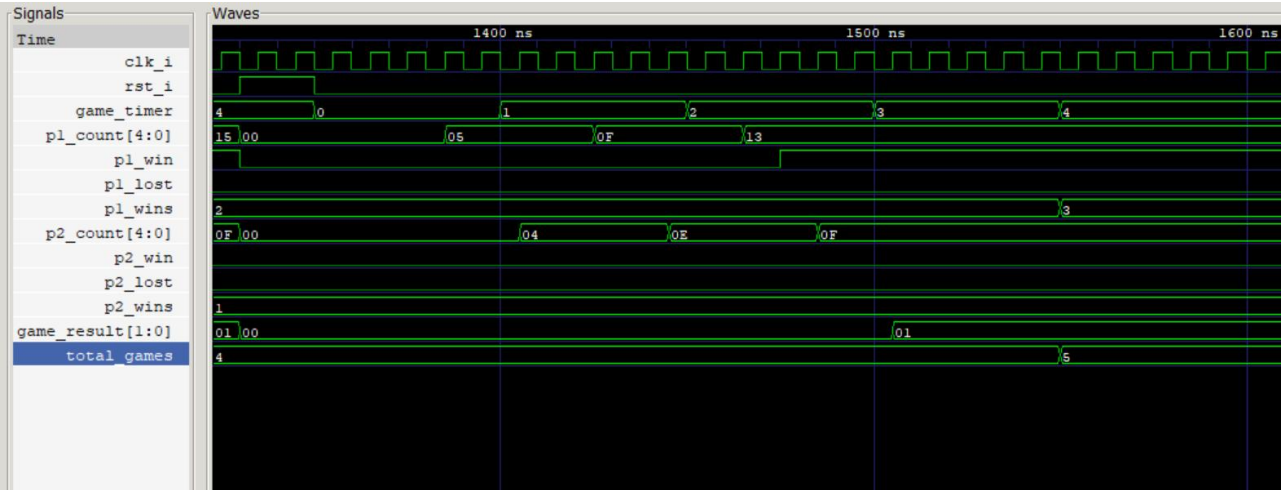

四、讨论与心得

我在 5.13 下午的课才了解到余锋老师更倾向于 ASM（Algorithmic State Machine）的状态转换图，所以吸取上一次实验使用 figma 的经验，修改了此次的 FSM 图。

总体而言，这次实验不仅巩固了我对有限状态机设计的理解，还提高了模块化设计能力和综合应用能力。通过扩展实现双玩家系统，我对复杂数字系统的分析和构建有了更全面的认识。通过对比单玩家和双玩家系统的不同，我也理解了系统复杂度增加时如何合理抽象和分解问题，裁判模块的设计让我学会了如何协调多个独立模块的工作。